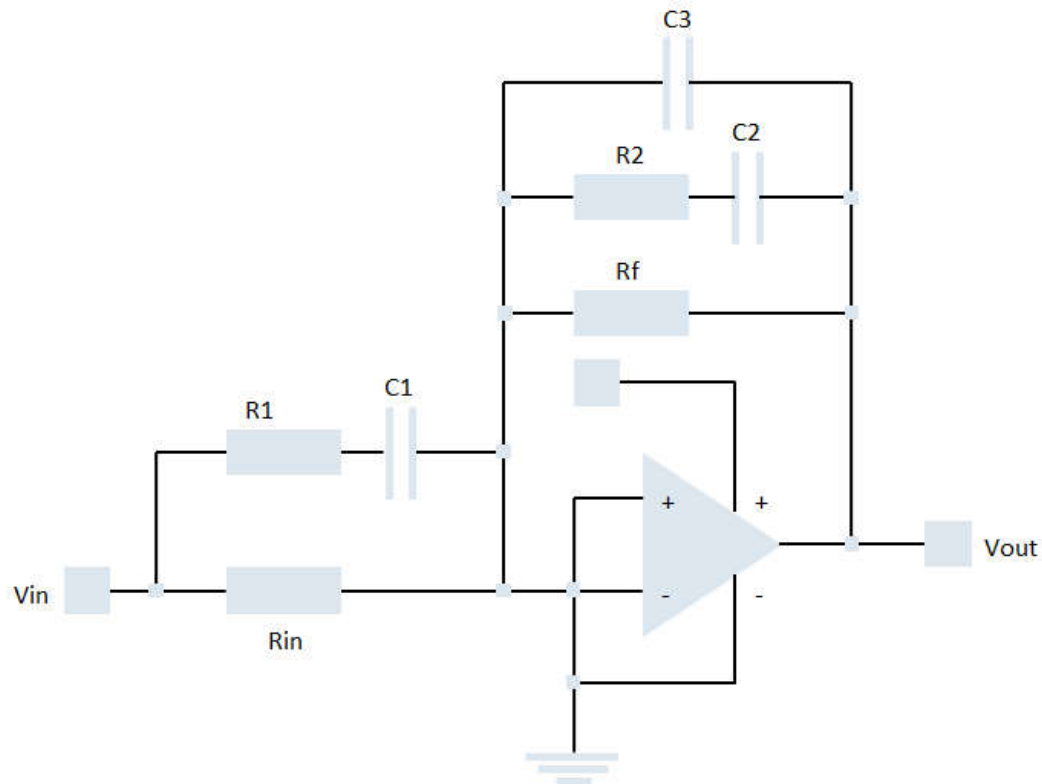


Amplifier Gain

▼ Introduction

In this application, we will plot the gain of the following amplifier circuit, for both the ideal and non-ideal response



```
> restart :  
with( DynamicSystems ) :  
with( plots ) :
```

▼ Parameters

```
> R1 := 1000 :  
> C1 := 10-7 :  
> Rin := 1000 :  
> C3 := 4.7 · 10-8 :  
> R2 := 1000 :  
> C2 := 4.70 · 10-7 :  
> Rf := 10102 :
```

Amplifier bandwidth factors

> GBP := 10^6 :

> LPF := 300 :

▼ Support Function

$$> \parallel := (Z_1, Z_2) \rightarrow \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} :$$

▼ Transfer functions

$$> Z_1 := R_1 + \frac{1}{s \cdot C_1} :$$

$$> Z_2 := R_2 + \frac{1}{s \cdot C_2} :$$

$$> Z_{in} := \parallel(R_{in}, Z_1) :$$

> factor(Z_{in})

$$\frac{500 (s + 10000)}{s + 5000}$$

$$> Z_{fb} := \parallel\left(R_f \parallel\left(Z_2, \frac{1}{s \cdot C_3}\right)\right) :$$

Ideal Amplifier Gain

$$> G_{EAideal} := \text{factor}\left(\frac{Z_{fb}}{Z_{in}}\right)$$

$$G_{EAideal} := \frac{42553.19148 (s + 2127.659574) (s + 5000.)}{(s + 1.934235977 \cdot 10^{-96}) (s + 23404.25531) (s + 10000.)}$$

Nonideal Op-Amp effects: Finite open loop gain

$$> \beta := \frac{1}{1 + G_{EAideal}} :$$

Finite open loop gain

$$> A_{vo} := \frac{GBP}{LPF} \cdot \frac{1}{\left(1 + \frac{s}{2 \cdot \pi \cdot LPF}\right) \cdot \left(1 + \frac{s}{2 \cdot \pi \cdot GBP}\right)}$$

$$A_{vo} := \frac{10000}{3 \left(1 + \frac{1}{600} \frac{s}{\pi}\right) \left(1 + \frac{1}{2000000} \frac{s}{\pi}\right)}$$

$$\text{> simplify} \left(A_{vo} := \frac{10000}{3 \left(1 + \frac{1}{600} \frac{s}{\pi} \right) \left(1 + \frac{1}{2000000} \frac{s}{\pi} \right)}, 'size' \right)$$

$$\frac{4000000000000 \pi^2}{(600 \pi + s) (2000000 \pi + s)}$$

Nonideal error amplifier gain

$$\text{> } G_{EA} := \text{simplify} \left(G_{EAideal} \cdot \frac{1}{1 + \frac{1}{A_{vo} \cdot \beta}} \right)$$

$$G_{EA} := (42553.19148 (s + 5000.) (s + 2127.659574)) / (1.012406241 s^3 + 33512.60113 s^2 + 2.342758273 10^8 s + 1.358080578 10^8 + 1.611267141 10^{-7} s^4 + 2.53302959 10^{-14} s^5)$$

▼ Analysis

> with(DynamicSystems) :

> sys1 := TransferFunction(G_{EA}) :

> sys2 := TransferFunction($G_{EAideal}$) :

> p1 := PhasePlot(sys1, range = 10 ..100000, hertz = true, legend = "Non-ideal") :

> p2 := PhasePlot(sys2, range = 10 ..100000, hertz = true, legend = "Ideal" , color = black) :

> display(p1, p2)

