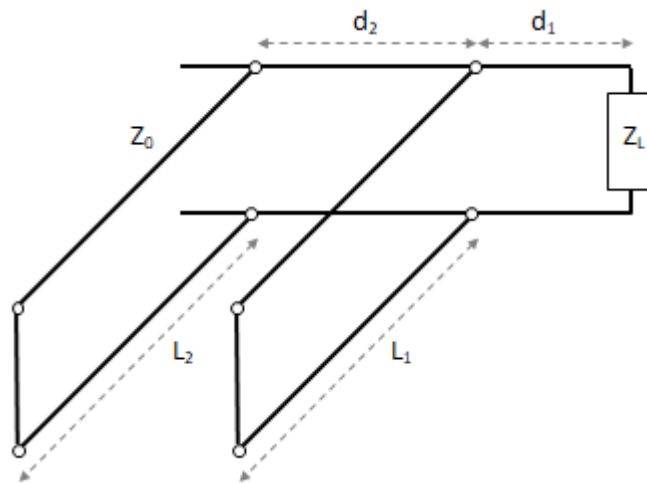


Double Stub Matching

This application will calculate the lengths L_1 and L_2 of two shunt stubs that match the load to the impedance of a transmission line.

The shunts are at a known position d_1 and d_2 from the load.



Parameters

Load and impedance	$Z_L := (23 - 38i) \text{ ohm}$	$Z_0 := 100 \text{ ohm}$
Wavelength and phase constant	$\lambda := 1 \text{ m}$	$\beta := \frac{2 \cdot \pi}{\lambda} = 6.283 \frac{1}{\text{m}}$
Position of stubs	$d_1 := 0.26 \cdot \lambda$	$d_2 := 0.18 \cdot \lambda$

Circuit equation

$$\text{circuit} := \frac{\cos(\beta \cdot d_2) + \frac{1 \cdot i \cdot \sin(\beta \cdot d_2)}{\frac{Z_0 \cdot \cos(\beta \cdot d_1) + 1 \cdot i \cdot Z_L \cdot \sin(\beta \cdot d_1)}{Z_L \cdot \cos(\beta \cdot d_1) + 1 \cdot i \cdot Z_0 \cdot \sin(\beta \cdot d_1)} - 1 \cdot i \cdot \cot(\beta \cdot L_1)}}{\frac{\cos(\beta \cdot d_2)}{\frac{Z_0 \cdot \cos(\beta \cdot d_1) + 1 \cdot i \cdot Z_L \cdot \sin(\beta \cdot d_1)}{Z_L \cdot \cos(\beta \cdot d_1) + 1 \cdot i \cdot Z_0 \cdot \sin(\beta \cdot d_1)} - 1 \cdot i \cdot \cot(\beta \cdot L_1)} + 1 \cdot i \cdot \sin(\beta \cdot d_2)} - 1 \cdot i \cdot \cot(\beta \cdot L_2)}$$

Analysis

Numerical solution

$\text{res} := \text{fsolve}(\{\text{Re}(\text{circuit}) = 1, \text{Im}(\text{circuit}) = 0\},$
 $\{L_1 = 0.1 \text{ m}, L_2 = 0.1 \text{ m}\})$ assuming real

$\text{res} = \{L_1 = 0.298 \text{ m}, L_2 = 0.086 \text{ m}\}$